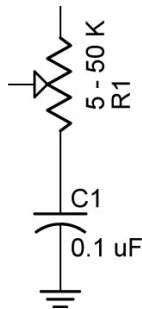


Electronics and Robotics I Week 25


Resistive Sensors

- **Administration:**
 - Prayer
- **PicBasic Pro Programs Used in This Lesson:**
 - General PicBasic Pro Program Listing:
<http://www.cornerstonerobotics.org/picbasic.php>
 - Lab 1 adc1 as a .pdf file:
<http://www.cornerstonerobotics.org/code/adc1.pdf>
 - Lab 1 adc2 as a .pdf file:
<http://www.cornerstonerobotics.org/code/adc2.pdf>
 - Lab 1 adc3 as a .pdf file:
<http://www.cornerstonerobotics.org/code/adc3.pdf>
 - Lab 2 braitenberg1 as a .pdf file:
<http://www.cornerstonerobotics.org/code/braitenberg1.pdf>
 - Lab 3 bend_sensor1.pbp as a .pdf file:
http://www.cornerstonerobotics.org/code/bend_sensor1.pdf
- **Resistive Sensors:**
 - **PicBasic Pro POT vs. ADCIN Commands:**
 - Depending upon the circuit conditions, resistive sensors may be read using the POT or ADCIN commands.
 - POT Command:
 - Resistive device normally within the 5 – 50 K ohm range.
 - The POT command measures the time it takes to charge a capacitor in a resistor/capacitor series circuit. Knowing the value of the capacitor and the charging time, the PIC converts the time value into an 8-bit resistance value of 0 - 255.
 - There is no voltage source when using the POT command therefore it does not measure a voltage drop. See the schematic comparison below.
 - Restricted to an 8-bit variable, giving outputs from 0 – 255.
 - See the following website for further discussion:
<http://books.google.com/books?id=XYwuCq5u2oEC&pg=PA189&lpg=PA189&dq=resistive+sensors+picbasic+pro&source=web&ots=d9Vra7g0Z2&sig=dZ5MI3R4vSSOCE9aeaxEronc8gw>

- ADCIN Command:
 - ADCIN, which reads an A/D converter (analog to digital converter), measures a voltage drop across a resistor.
 - There is a voltage source when using the A/D command ADCIN.
 - Variables may be 8, 10, or 12-bit, generating outputs of 0 – 255, 0 – 1024, or 0 – 4096 respectfully. The ADCIN command is more accurate than the POT command.



POT Uses No Voltage Source

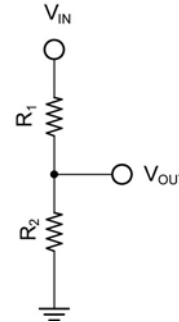


ADCIN Has a Voltage Source, V_{IN}

- This lesson will focus on the ADCIN command.

○ **Voltage Divider Review:**

- Voltage at Point A, V_A :

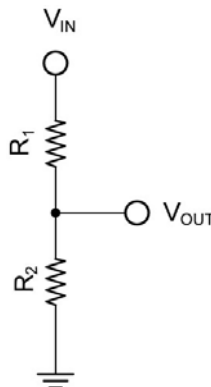

- Current through the series resistors:

$$V_{IN} = I R_{TOTAL}, \text{ since } R_{TOTAL} = R_1 + R_2,$$


$$V_{IN} = I (R_1 + R_2)$$

Solving for I,

$$I = V_{IN} / (R_1 + R_2)$$

- V_{OUT} :
 $V_{OUT} = I R_2$, since the current, I , was solved above,
 $V_{OUT} = [V_{IN} / (R_1 + R_2)] \times R_2$, and
 $V_{OUT} = V_{IN} \times R_2 / (R_1 + R_2)$
- Cases:
 - When R_2 equals R_1 , then V_A equals $\frac{1}{2} V_{IN}$.
 - When R_2 is smaller than R_1 , then V_{OUT} will be closer to 0 volts or ground; conversely, when R_2 is larger than R_1 , then V_{OUT} will be closer to V_{IN} .
- In our application, $V_{IN} = +5V$, so V_{OUT} varies from near 0 V to near +5 V.

- Perform Resistive Sensors LAB 1 – Reading a Potentiometer
- **Photoresistor Sensors (Cadmium Sulfide, CdS, Photo Sensor):**
 - Cadmium sulfide changes in resistance when exposed to varying degrees of light. The resistance of a CdS photoresistor or photocell decreases as it receives more light (an inverse relationship).
 - Photocells have a relatively slow response to changes in light. The characteristic blinking of overhead fluorescent lamps, which turn on and off at the 60 Hertz line frequency, is not detected by photocells.
 - Demonstrate 60 Hz frequency using a photocell and phototransistor circuits and a frequency counter and oscilloscope. Video?
 - If a photoresistor is substituted for R_2 in the voltage divider above and it is illuminated brightly, its resistance will be low and V_A will be near 0V.
 - In contrast, if the same photoresistor is shielded from light, its resistance will be high and V_A will be near +5V.
 - Photoresistors normally require shielding because they are sensitive to ambient or surrounding light.
 - Use the photoresistor as R_2 in the voltage divider. See below:

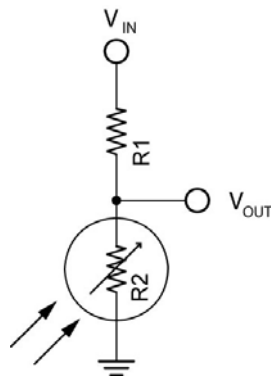

CdS Photocell in Voltage Divider

- Use the following formula to calculate the value for R_1 :

$$R_1 = \text{SQRT}(\text{CdS}_{\text{DARK}} * \text{CdS}_{\text{BRIGHT}})$$

Where:

R_1 = Resistance of Resistor 1,
 CdS_{DARK} = Resistance of the CdS photocell in the darkest condition the photocell will operate,
 $\text{CdS}_{\text{BRIGHT}}$ = Resistance of the CdS photocell in the brightest condition the photocell will operate

- Source and derivation of the equation:
http://www.societyofrobots.com/schematics_photoreistor.shtml
- Complete Resistive Sensors LAB 2 – CdS Photoresistors
- **Other Resistive Sensors:**
 - Bend Sensors:
 - The resistance of the sensor increases in proportion to the degree of bending or flexing. For the Jameco #150551, 0 degrees is about 10K ohms and 90 degrees is 30K – 40K ohms.
 - Perform Resistive Sensors Lab 3 – Bend Sensors
 - Source for bend sensors:
<http://www.robotshop.ca/home/products/robot-parts/sensors/stretch-bend-sensors/>

Electronics and Robotics I Week 25 Resistive Sensors LAB 1 – Reading a Potentiometer

- **Purpose:** The purpose of this lab is to teach the student how to wire a PIC18F88 for analog/digital conversion, to expose the student to the PicBasic Pro command ADCIN, and to introduce the linear slide sensor.


- **Apparatus and Materials:**

- 1 – Breadboard with +5V supply or an Analog/Digital Trainer
- 1 – PIC 16F88 Microcontroller
- 1 – 10 K Tripot
- 1 – Phidgets Slide Sensor, Product # RB-Phi-20 from:

<http://www.robotshop.ca/home/products/robot-parts/sensors/linear-rotary-resistors/index.html>

- **Procedure:**

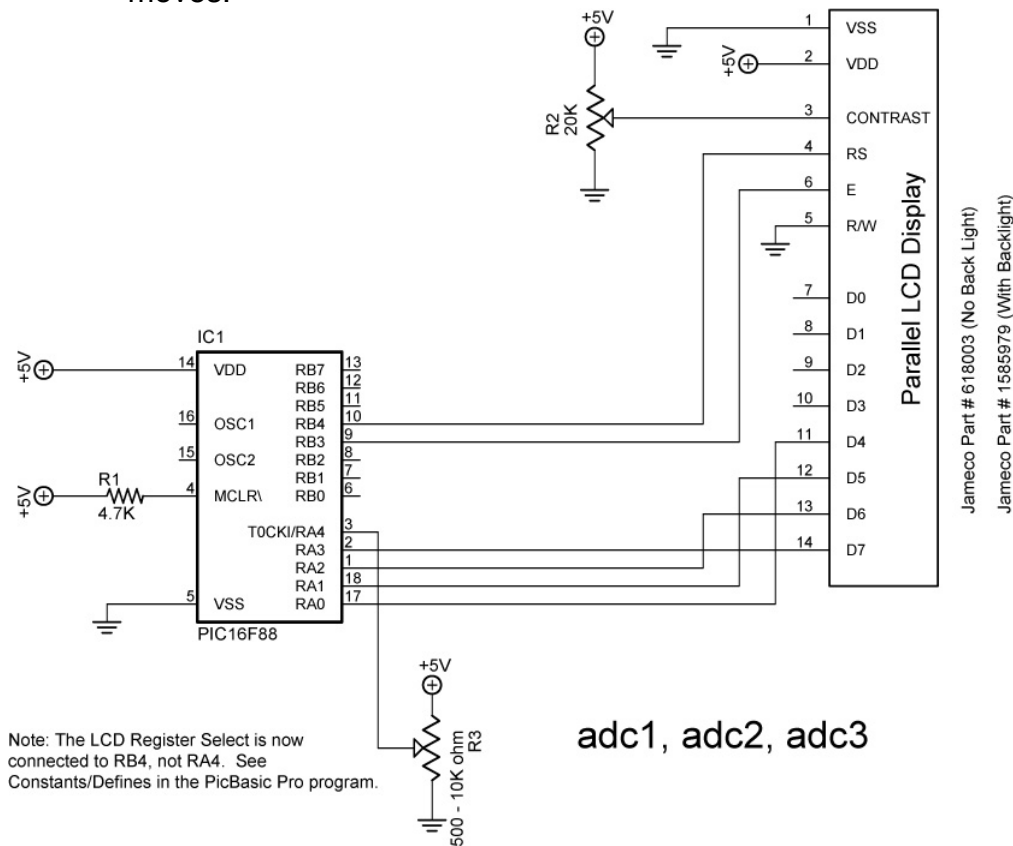- Wire the circuit below. Use a 10K tripot for R3. Make sure to read the note in the schematic.
- Program the PIC16F88 with **adc1.pbp**, **adc2.pbp**, and then **adc3.pbp**. Adjust R3 and note the values on the LCD screen for each program.
- Now substitute the slide sensor for the 10K tripot. Note the changes in the LCD value as the linear position of the slide sensor moves.




Electronics and Robotics I Week 25 Resistive Sensors LAB 2 – CdS Photoresistors

- **Purpose:** The purpose of this lab is to acquaint the student with the use of a CdS photocell as a resistive sensor.

- **Apparatus and Materials:**
 - 1 – Robotic Car Platform
 - 1 – PIC 16F88 – I/P Microcontroller
 - 1 – LCD Screen, Jameco #618003
 - 1 – 20 K Ohm Potentiometer
 - 2 – CdS Photoresistors, Jameco #120299 (300K-Dark, 8K-Light)
 - 1 – 4.7K Resistor
 - 4 – 1K Resistor, Includes R3 and R8
 - 2 – 2N2222A NPN Transistors


- **Procedure:**
 - Wire the following circuit.
 - Program the PIC16F88 with **braitenberg1.pbp**.
 - Adjust the CdS photocells for the car to be attracted to the light.
See: http://www.youtube.com/watch?v=N_X4_VVxOrE


- **Challenges:**
 - **Line-follower:** Mount CdS sensors on your robotic car for the car to follow a taped line. See: <http://www.youtube.com/watch?v=ut0iTLZykog>
 - **Light-Steering:** Use one photocell to activate steering or forward motion for the robotic car. Use a second photocell to turn the robotic car off. The car must begin in the starting box and come to a complete stop in the finish box.
 - **CdS switch:** Wire a circuit and program a PIC16F88 to serve as a light activated switch which turns on and off an LED.

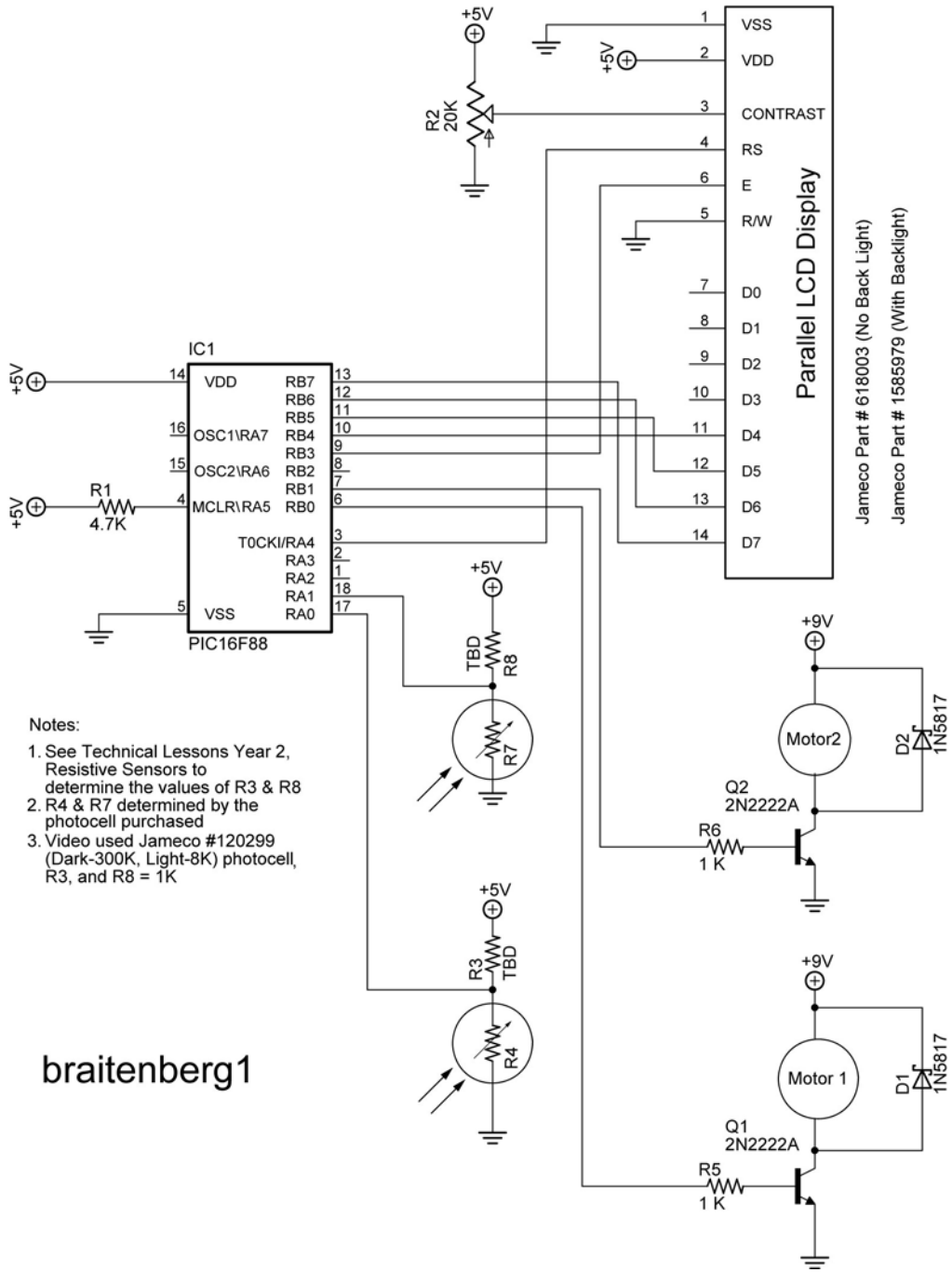

Electronics and Robotics I Week 25 Resistive Sensors LAB 3 – Bend Sensors

- **Purpose:** The purpose of this lab is to acquaint the student with the function of a bend sensor.
- **Apparatus and Materials:**
 - 1 – Breadboard
 - 1 – PIC 16F88 Microcontroller
 - 1 – 4.7K Ohm Resistor
 - 1 – 22K Resistor
 - 1 – 20K Tripot
 - 1 – Bend Sensor, Jameco #150551
 - 1 – LCD Screen, Jameco # 618003
 - 1 – Futaba 3003 Hobby Servo
- **Procedure:**
 - Wire the circuit bend_sensor1.
 - Program the PIC16F88 with **bend_sensor1.pbp**
 - Bend flex sensor and note servo movement.
 - Review the derivation of the equation in the graph below.

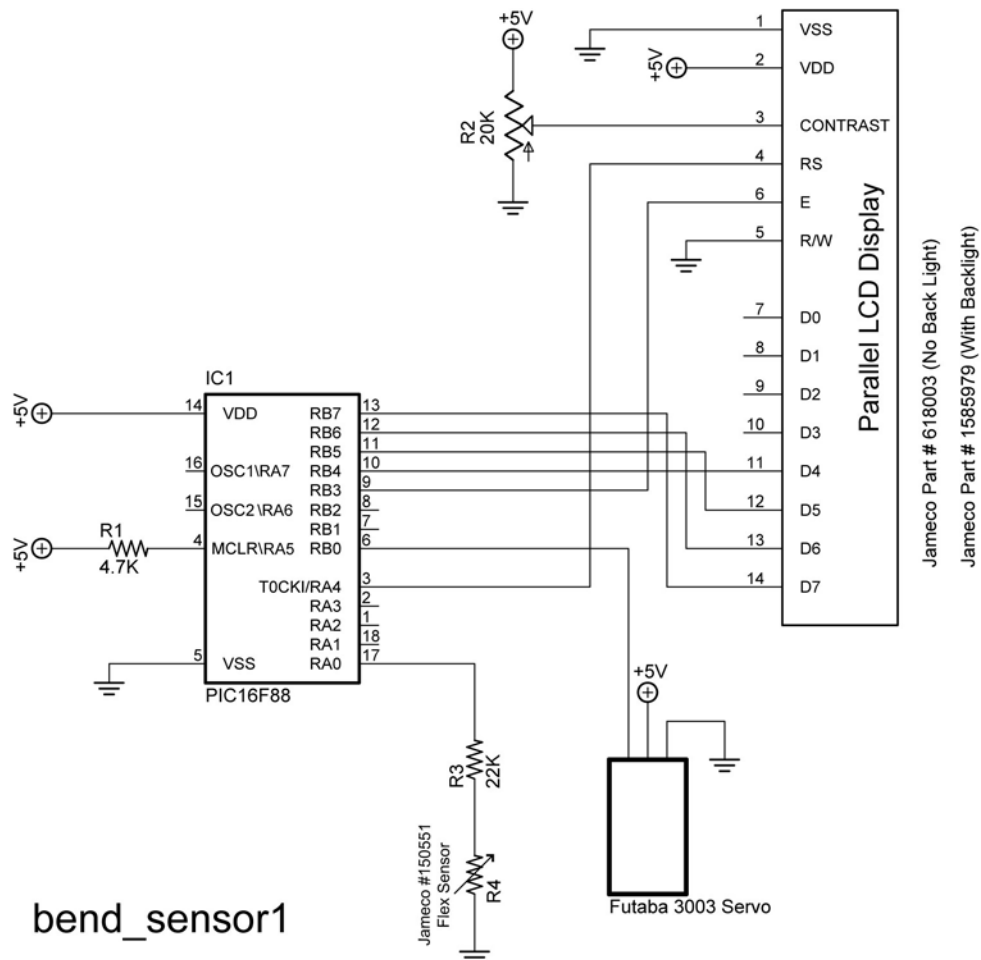

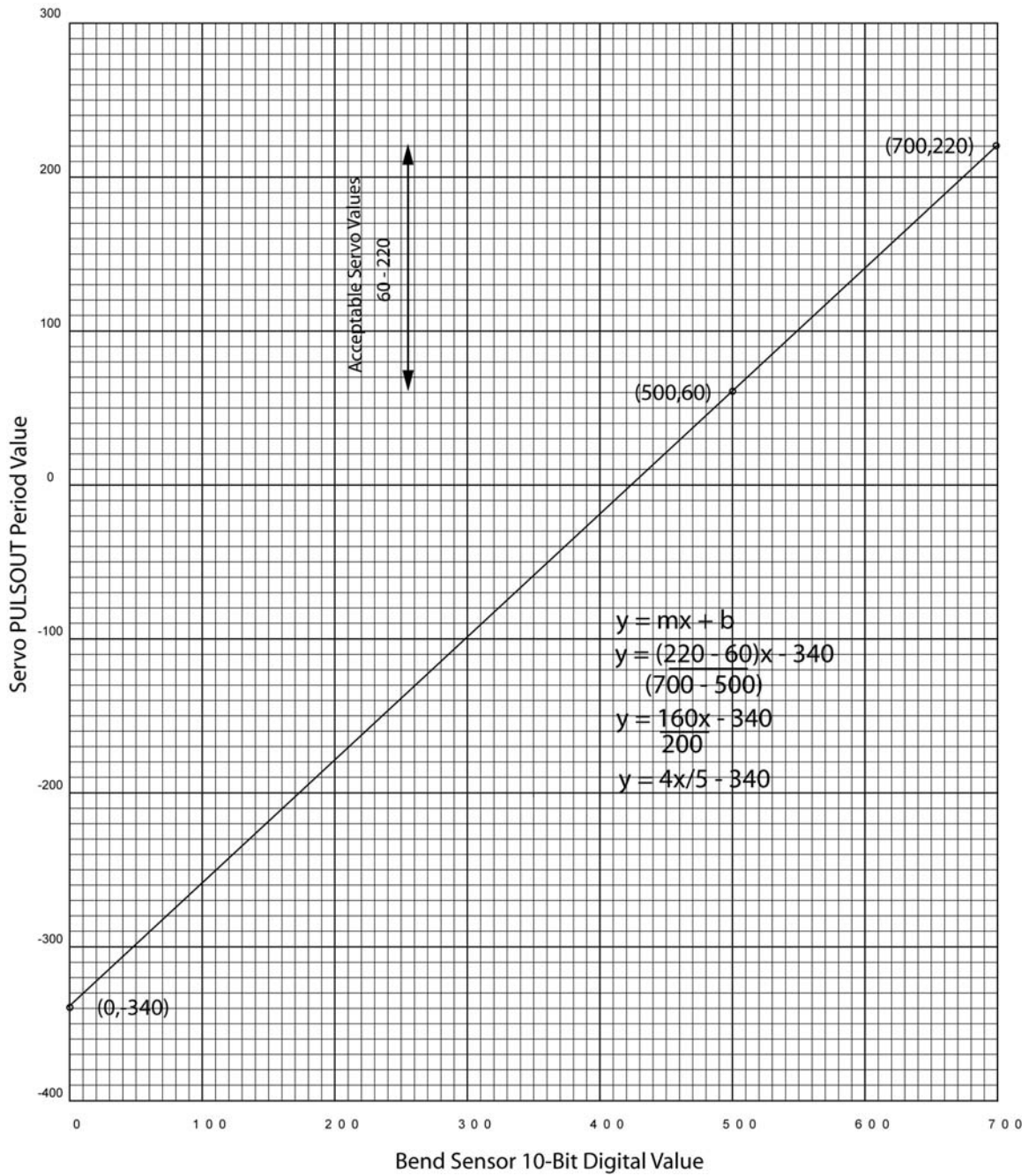

Derivation of Formula Used in bend_sensor1.pbp