

Electronics Technology and Robotics I Week 9

Electrical Relays

- Administration:
 - Prayer
 - Using a LM393 and a flashlight acting as the sun, design and construct a circuit that turns off an LED “streetlight” when the sun rises.
 - Review voltage regulators:



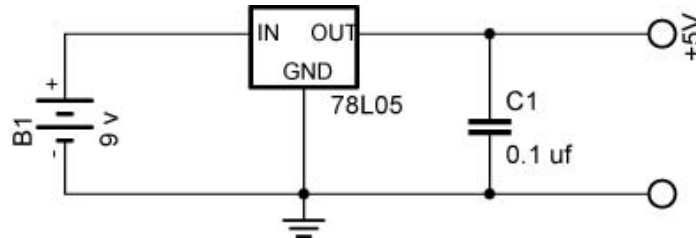


Figure 1: 78L05 Voltage Regulator Circuit

- Review SPST, SPDT, DPST, DPDT switches
http://cornerstonerobotics.org/curriculum/lessons_year1/ER%20Week8,%20Switches,%20Fuses.pdf
- Electricity and Electronics, Section 9.3, **Relays:**
 - Introduction: In many cases, it is impractical to use a manual switch in a circuit. For instance, you would not want to wait for the temperature in your house to rise above a certain level and then manually turn the air conditioning by throwing a manual switch. An automatic switching device would better serve the purpose.
 - General: A relay is an electrically activated switch. It is a device that is used to control a large voltage, large current circuit by means of a low voltage, low current circuit.
 - Three Types of Relays:
 - Mechanical relays
 - High currents, slow switching speeds
 - Reed relays
 - Moderate currents, moderate switching speed
 - Can be damaged by power surges
 - Solid-state relays
 - Wide range of currents, very fast switching speeds
 - Can be damaged by power surges
 - Major Parts of a Mechanical Relay (See Figures 2 and 3):
 - Coil which serves as an electromagnet
 - Armature – the lever arm
 - Contact points
 - Spring

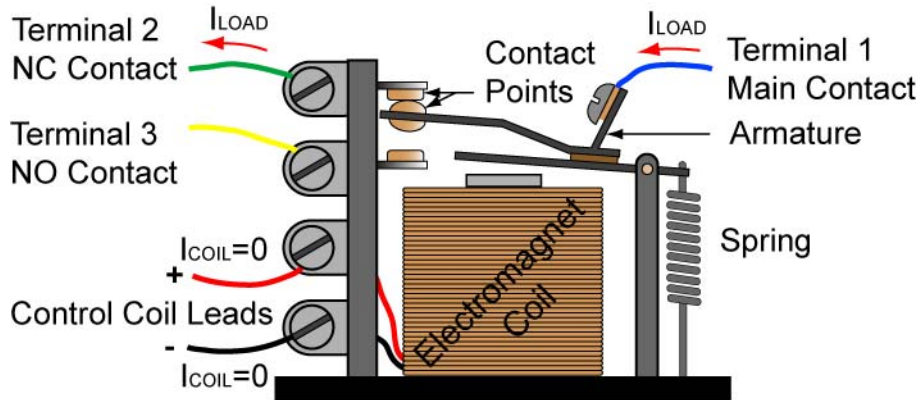

**Figure 2: De-energized SPDT Relay – Spring Holds Armature in Position
Continuity from Terminal 1 (Main Contact) to Terminal 2 (NC Contact)**

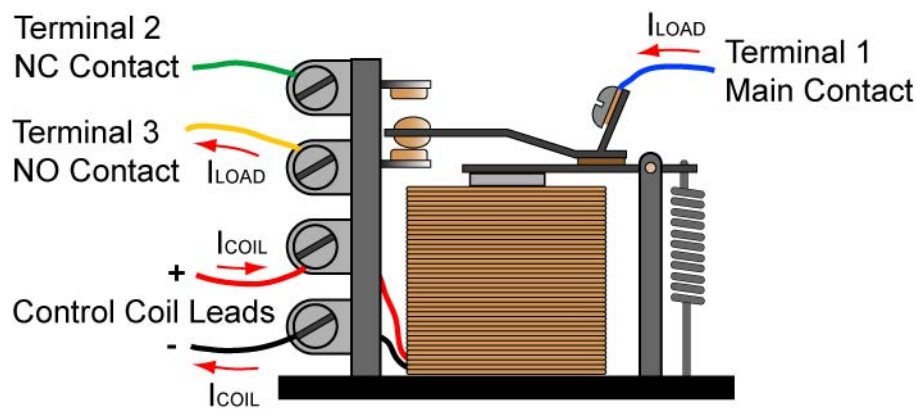

**Figure 3: Energized SPDT Relay – Electromagnet Pulls Armature into Other Position
Continuity from Terminal 1 (Main Contact) to Terminal 3 (NO Contact)**

- Action: When the control circuit of a relay energizes the coil, the coil's attraction force pulls a lever arm called an armature toward the coil. This action turns the secondary circuit on and off. See Figures 4 and 5.

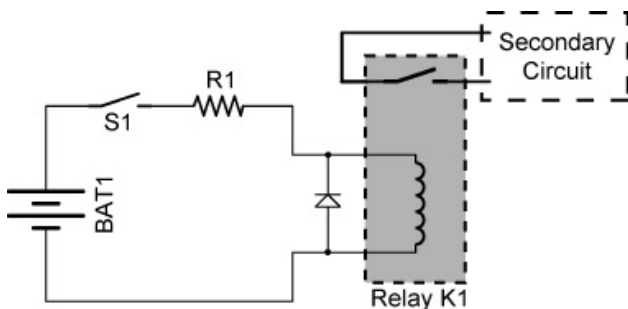


Figure 4: De-energized Relay
With S1 open, the relay coil is not energized and the relay K1 switch remains open.

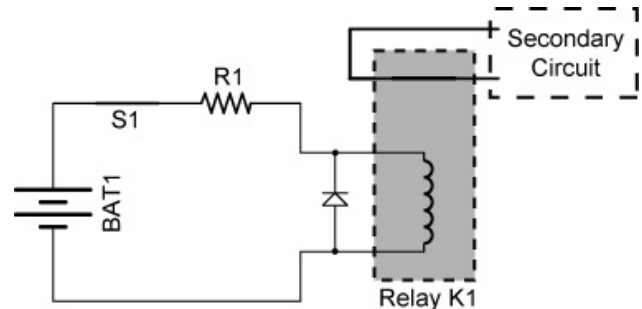


Figure 5: Energized Relay
S1 is closed and the relay coil is energized. This causes switch in the relay K1 to close, turning on the secondary circuit.

- The two different voltages can be connected mechanically by a relay. They are not connected electrically.

- Schematic Symbols:

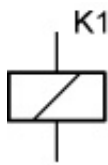


Figure 6: SPST Relay

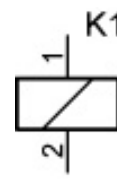
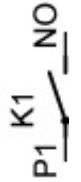


Figure 7: SPDT Relay

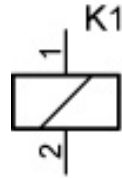
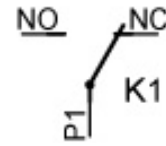


Figure 8: DPST Relay


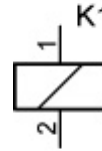
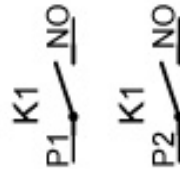
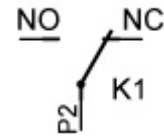


Figure 9: DPDT Relay

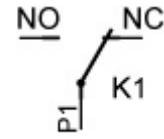

- Show samples
- Perform Electrical Relays Lab 1 – Voltage Separation
- Normally Open (NO) and Normally Closed (NC) Relays:
 - NO/NC relays are similar to NO/NC switches in their operation.
 - NC relays are closed when the relay coil is de-energized.
 - NO relays are open when the relay coil is de-energized.
 - SPDT & DPDT relays have both NO & NC contacts.
 - See: <http://tams-www.informatik.uni-hamburg.de/applets/hades/webdemos/05-switched/20-relays/relay.html>
- Just as a SPDT switch can act as a SPST switch, a SPDT relay can serve as a SPST relay by not making connection to one of the contacts.
- Advantages:
 - An electrical equipment operator is exposed to lower, safer control voltages rather than high equipment voltages.
 - Equipment can be controlled from remote locations.
 - Smaller wires can be run from the control room to the equipment.
 - Relays can have a rapid switching action.
- Using Relays vs. Transistor Switches:
 - Transistors cannot switch AC or high voltages (such as mains electricity) and they are not usually a good choice for switching large currents (> 5A).
 - Advantages of relays compared to a transistor:
 - Relays can switch AC and DC, transistors can only switch DC.
 - Relays can switch high voltages, transistors cannot.
 - Relays are a better choice for switching large currents (> 5A).
 - Relays can switch many contacts at once.

- Disadvantages of relays compared to a transistor:
 - Relays are bulkier than transistors for switching small currents.
 - Relays cannot switch rapidly; transistors can switch many times per second.
 - Relays use more power due to the current flowing through the coil.
 - Relays require more current than many ICs can provide, so a low power transistor may be needed to switch the current for the relay's coil.

(Relay/transistor comparison from: <http://www.kpsec.freeuk.com/trancirc.htm>)

○ Notes:

- The voltage across the relay coil should be within 25% of the relay specification.
- If current flow through a relay coil is suddenly interrupted, the coil will produce a very large voltage spike in the reverse direction of the applied voltage. To handle these reverse voltage spikes, place a transient suppressor diode across the relay's coil.


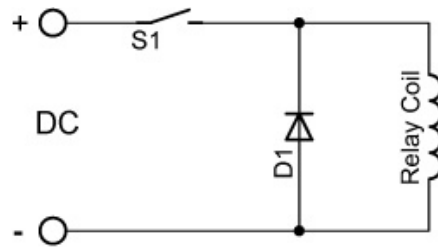


Figure 10: Transient Suppressor Diode D1 for a DC Driven Relay Coil


- Perform Electrical Relays Lab 2 – Relay Application 1
- Reed Relays:
 - External permanent magnet or electromagnet
- Perform Electrical Relays Lab 3 – Controlling a DC Motor Direction with Relays

Electronics Technology and Robotics I Week 9 Electrical Relays Lab 1 – Voltage Separation


- **Purpose:** The purpose of this lab is to demonstrate that the voltage source which controls a relay coil can be separate from the voltage source that controls the secondary circuit.
- **Apparatus and Materials:**
 - 1 – Breadboard with a +5 V and +9 V Power Supplies
 - 1 – 1N4004 Diode
 - 1 – SPST Relay (Digikey # Z945-ND)
<http://search.digikey.com/scripts/DkSearch/dksus.dll?Detail?name=Z945-ND>
 - 1 – SPST Switch
 - 1 – 1K Resistor
 - 1 – LED
- **Procedure:**
 - Build Relay Circuit 1 on your breadboard. The circuit uses a voltage source of +5 V to energize the relay coil and a separate a voltage source of +9 V to power the LED circuit.
 - Notice that the two circuits in Relay Circuit 1 are not connected electrically. Their interaction is by the coil generating a magnetic field which closes the contacts (switch) in the relay.

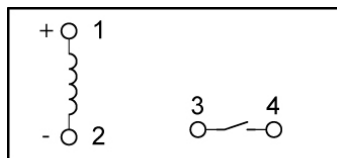

K1 (Z945-ND Top View)

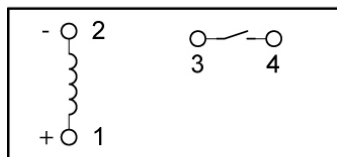

K1 (Z945-ND Bottom View)

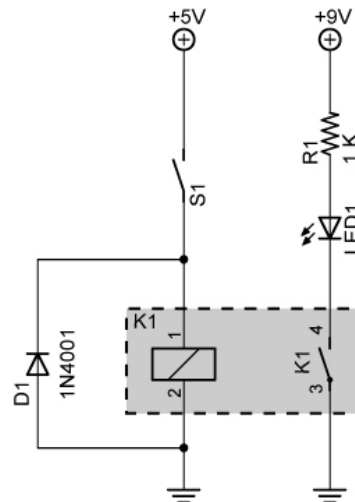

Relay Circuit 1

SPST Relay Wiring Diagram

- **Results:**

| Position of Switch | LED Response |
|--------------------|--------------|
| S1 Open | |
| S1 Closed | |


- **Conclusions:**
 - The data sheet for the relay states, “When mounting two or more relays side by side, provide a minimum space of 3 mm between relays.” Why?

Electronics Technology and Robotics I Week 9 Electrical Relays Lab 2 – Relay Application 1


- **Purpose:** The purpose of this lab is to demonstrate an application of a relay.
- **Apparatus and Materials:**
 - 1 – Breadboard with a +5V and +9V Power Supply
 - 1 – 1 K Tripot
 - 1 – Photoresistor
 - 1 – 4.7 K Resistor
 - 2 – 1 K Resistors
 - 1 – 2N2222A NPN Transistor
 - 1 – 1N4001 Diode
 - 1 – LED
 - 1 – SPST Relay (Digikey # Z945-ND)

<http://search.digikey.com/scripts/DkSearch/dksus.dll?Detail?name=Z945-ND>

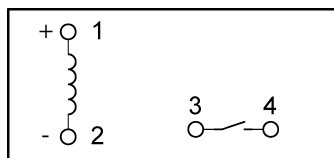- **Procedure:**
 - Wire the following light activated relay circuit:




K1 (Z945-ND Top View)

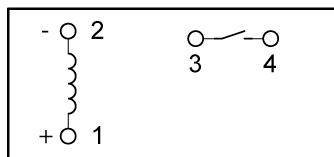

K1 (Z945-ND Bottom View)


SPST Relay Wiring Diagram

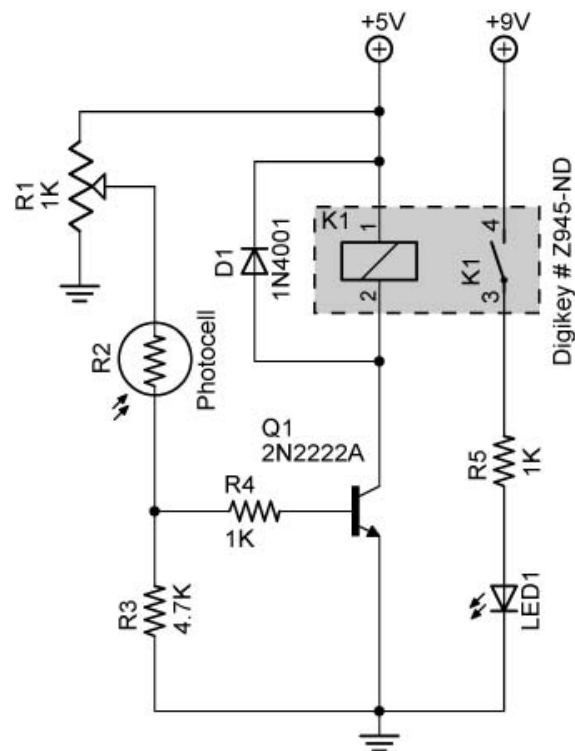


Light Activated Relay Circuit

Electronics Technology and Robotics I Week 9 Electrical Relays Lab 3 – Controlling a DC Motor Direction with Relays

- **Purpose:** To demonstrate how relays can be used to control the polarity of a dc motor.
- **Apparatus and Materials:**
 - 1 – Breadboard with a +5V and +12V Power Supply
 - 1 – 12V DC Motor (Jameco #155855 or similar)
 - 2 – 1N5817 Schottky Diodes
 - 2 – SPDT DC Reed Relays 5V DC Coil Voltage, (Digi-Key #HE112-ND)
 - Source: http://www.digikey.com/scripts/DkSearch/dksus.dll?WT.z_header=search_go&lang=en&keywords=he112-nd&x=0&y=0&cur=USD
 - Datasheet (Part #HE721C0500): <http://www.hamlin.com/specsheets/HE700.pdf>
- **Procedure:**
 - Build the circuit below:
 - Turn Switches S1 and S2 ON and OFF and fill in the table in results.

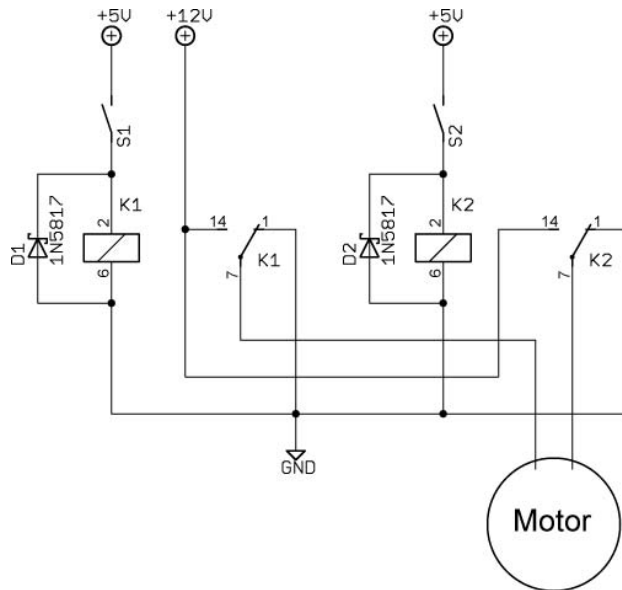

Motor Control Using Two SPDT Relays

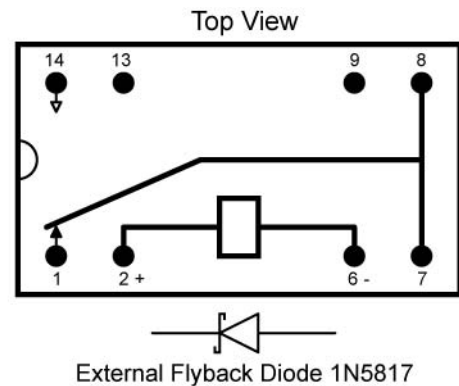


Pinout for SPDT Reed Relay

- **Results:**


| Motor Relay Logic | | |
|-------------------|---------|--------------|
| Relay 1 | Relay 2 | Motor Status |
| | | |
| | | |
| | | |
| | | |

- **Conclusions:**

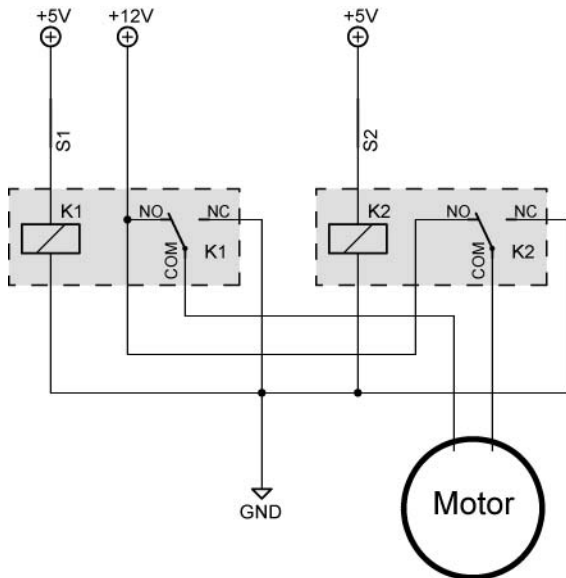
- Using arrows to represent current, draw the current through the relays and motor in each schematic below. Also show the polarity at the motor terminals and the direction of the motor rotation. If there is no current, just show the polarity at the motor terminals.




S1 and S2 Closed, Relays 1 and 2 ON

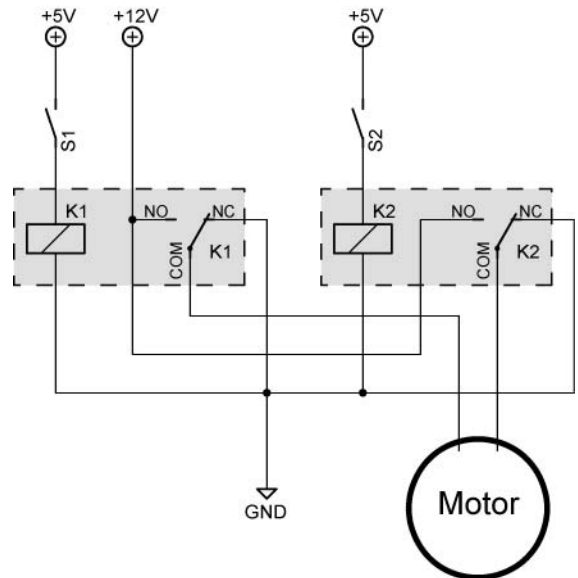

S1 and S2 Open, Relays 1 and 2 OFF

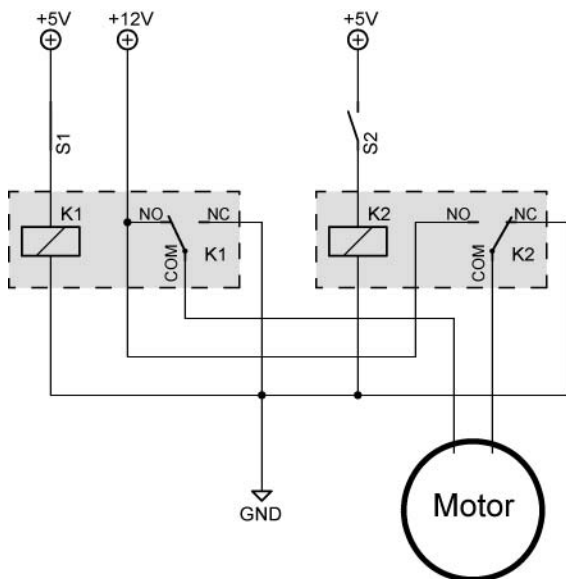


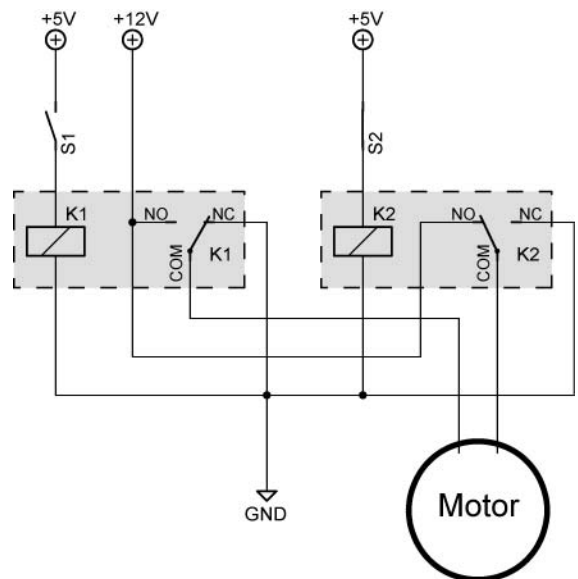**S1 Closed, S2 Open,
Relay 1 ON, Relay 2 OFF**




**S1 Open, S2 Closed,
Relay 1 OFF, Relay 2 ON**


• **Answers:**

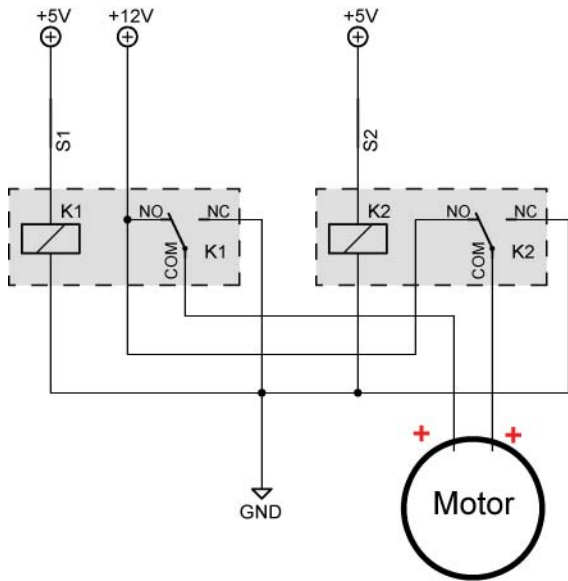


S1 and S2 Closed, Relays 1 and 2 ON

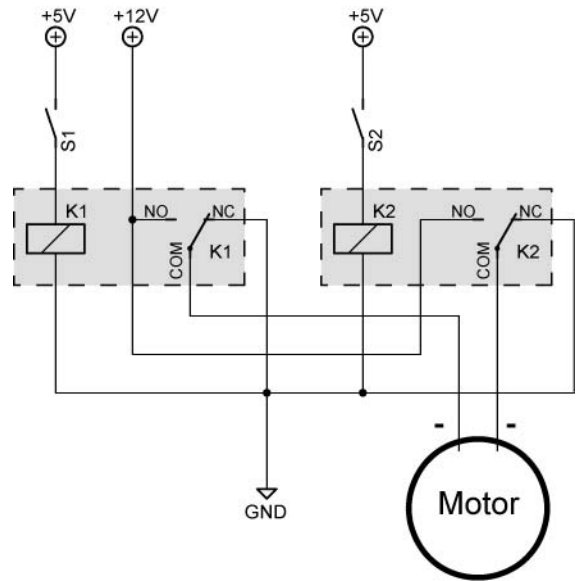

S1 and S2 Open, Relays 1 and 2 OFF

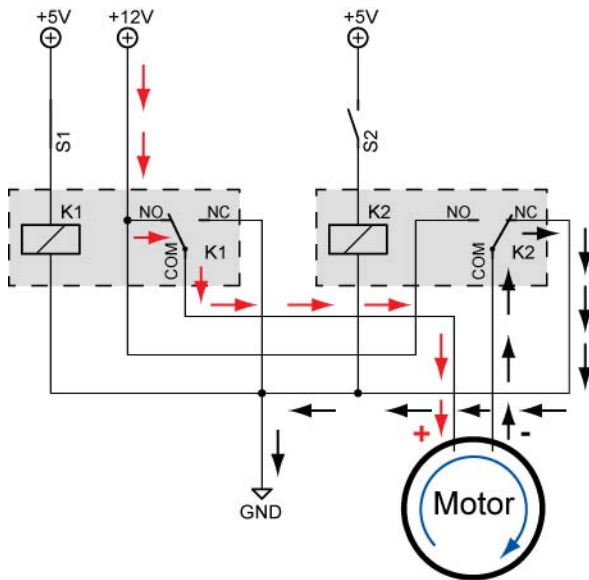

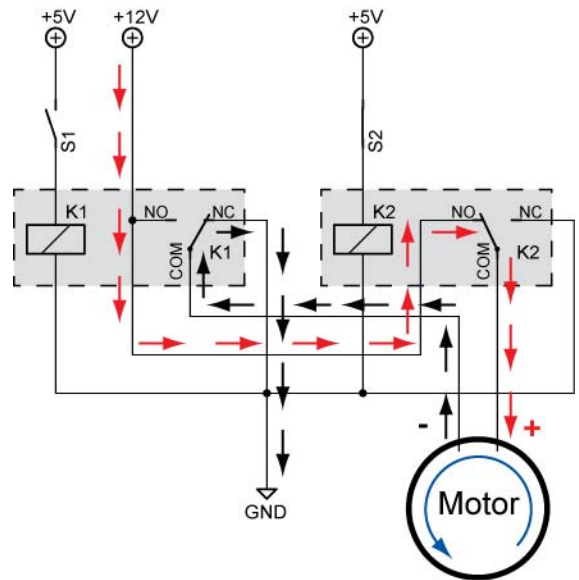**S1 Closed, S2 Open,
Relay 1 ON, Relay 2 OFF
(Rotation May Be Opposite)**



**S1 Open, S2 Closed,
Relay 1 OFF, Relay 2 ON
(Rotation May Be Opposite)**